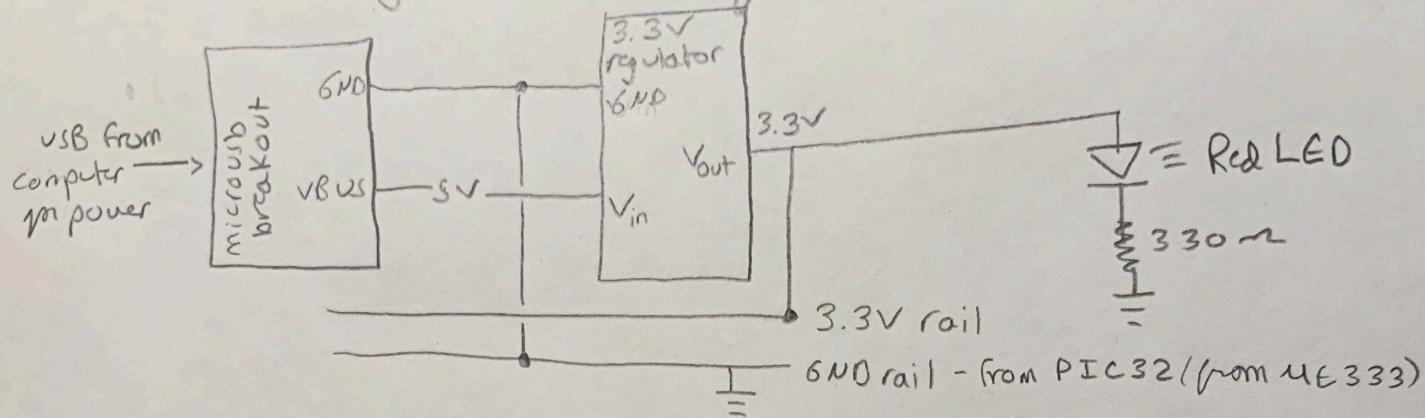
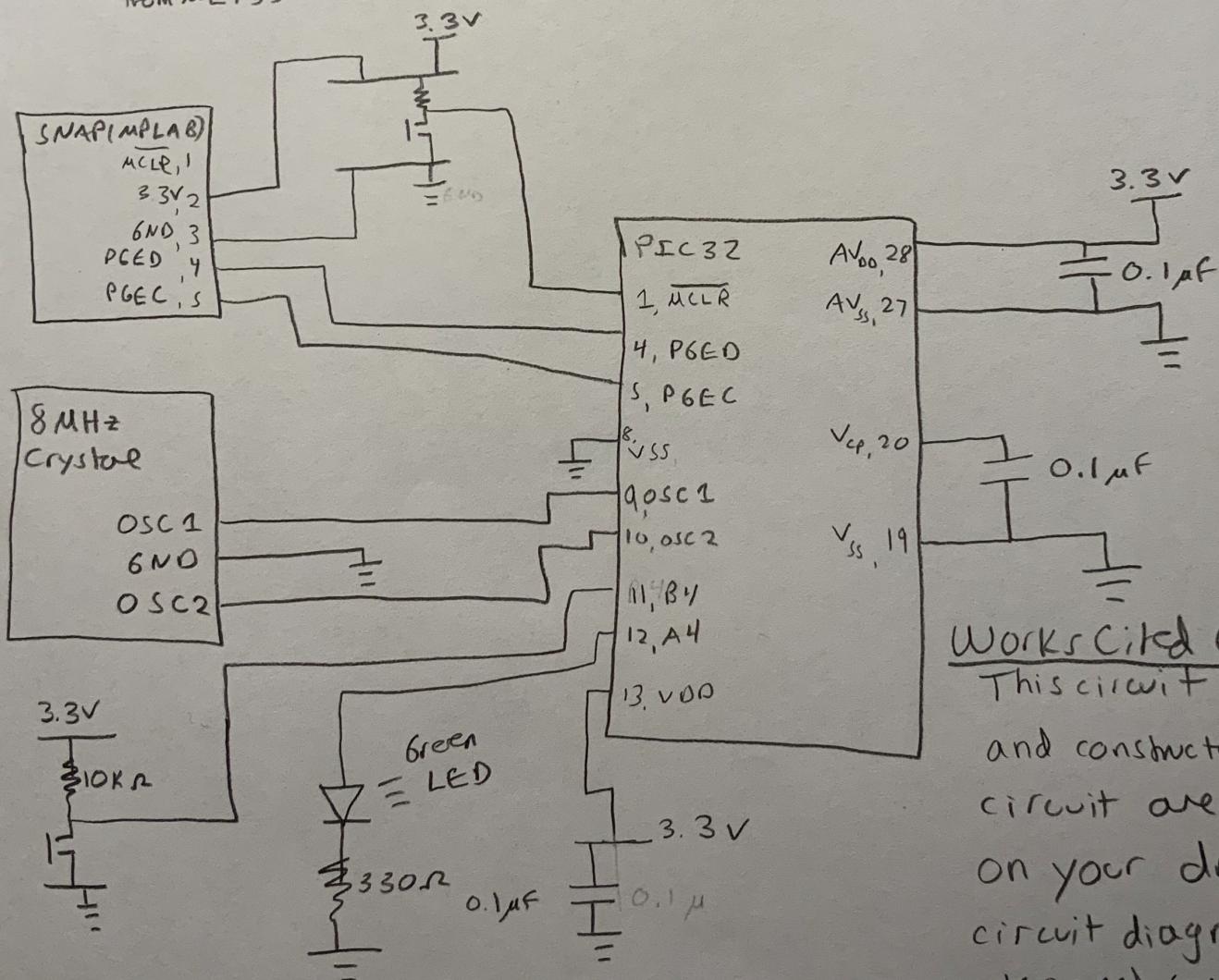


Power + Regulator (Source of all 3.3V sources)



PIC 32 Circuit (all 3.3V connections (μX170F256B) - from ME433



Works Cited (Note)
This circuit diagram
and constructed
circuit are based
on your drawn-out
circuit diagram. I
also used some of the
wiring techniques you used
in your completed circuit to
make mine neater. The
circuit built is a replica of
yours.